

## First-Order Differential Equations Review

We consider first-order differential equations of the form:

$$\frac{dx(t)}{dt} + \frac{1}{\tau}x(t) = f(t) \quad (1)$$

where  $f(t)$  is the forcing function. In general, the differential equation has two solutions:

1. *complementary* (or natural or homogeneous) solution,  $x_C(t)$  (when  $f(t) = 0$ ), and
2. *particular* (or forced or non-homogeneous) solution,  $x_P(t)$  (when  $f(t) \neq 0$ ).

In our problems,  $f(t)$  is often a constant, and therefore, the overall solution to the differential equation is

$$x(t) = x_C(t) + x_P(t) = K_1 e^{-t/\tau} + K_2 \quad (2)$$

The *time constant*,  $\tau$ , for first-order electrical circuits is either  $\tau = RC$  or  $\tau = L/R$ .

### Complementary Solution

The complementary solution is found by considering the *homogeneous equation*:

$$\frac{dx(t)}{dt} + \frac{1}{\tau}x(t) = 0 \quad (3)$$

The complementary solution is the system's *natural response*, which is

$$x_C(t) = K_1 e^{-t/\tau}$$

This result can be verified by substituting this answer into the differential equation, Eq. (3).

### Particular Solution

The particular solution is found by considering the full (non-homogeneous) differential equation, that is, Eq. (1). If the forcing function is a constant, then  $x_P(t)$  is a constant ( $K_2$ ) also, and hence  $\frac{dx_P}{dt} = 0$ . Substituting  $x_P$  into the original differential equation, Eq. (1), yields:

$$\frac{dx_P}{dt} + \frac{1}{\tau}x_P = 0 + \frac{1}{\tau}x_P = f$$

Reducing the above expression provides the particular solution, which is the *forced response*:

$$x_P = K_2 = \tau f$$

Note that, alternatively,  $K_2$  could have been found using Eq. (2) while considering the final value reached by the variable of interest, and hence, in this case is also the *steady-state response*:

$$x(\infty) = K_1 e^{-\infty} + K_2 = K_2$$

### Total Solution

The total solution is the sum of the complementary and particular solutions:

$$x_T(t) = x_C(t) + x_P = K_1 e^{-t/\tau} + \tau f \quad (4)$$

The coefficient term,  $K_1$ , is found from the initial conditions (at  $t = 0$ ).

### Initial Conditions

Typically, the initial conditions are determined by considering that for dc steady-state conditions:

(a) a capacitor is like an *open circuit* ( $i_C = C \frac{dv_C}{dt} = 0$ ), and (b) an inductor appears as a *short*

*circuit* ( $v_L = L \frac{di_L}{dt} = 0$ ). Further, the current through an inductor and the voltage across a capacitor cannot change instantaneously, for example,  $i_L(0^-) = i_L(0^+)$  and  $v_C(0^-) = v_C(0^+)$ .

## Second-Order Differential Equations Review

The second-order differential equations of interest are of the form:

$$\frac{d^2 y}{dt^2} + 2\zeta \omega_0 \frac{dy}{dt} + \omega_0^2 y(t) = f(t) \quad (5)$$

where  $f(t)$  is the forcing function. Like the first-order case, this differential equation has two solutions: (1) *complementary* (or natural) solution,  $y_C(t)$  when  $f(t) = 0$ , and (2) *particular* (or forced) solution,  $y_P(t)$  when  $f(t) \neq 0$ . In our problems,  $f(t)$  is often a constant, and therefore, the overall solution to the differential equation is typically

$$y(t) = y_C(t) + y_P(t) = K_1 e^{s_1 t} + K_2 e^{s_2 t} + K_3 \quad (6)$$

### Complementary Solution

The complementary solution is found by considering the homogeneous equation:

$$\frac{d^2 y}{dt^2} + a \frac{dy}{dt} + b y(t) = 0 \quad (7)$$

where  $a = 2\zeta \omega_0$  and  $b = \omega_0^2$ . The complementary solution is the system's *natural response*:

$$y_C(t) = K_1 e^{s_1 t} + K_2 e^{s_2 t} \quad (8)$$

The *natural frequencies*,  $s_1$  and  $s_2$ , are the roots of the *characteristic equation*:

$$s^2 + a s + b = 0 \quad (9)$$

These roots lead to three possible cases:

$\zeta$	Roots ( $s_1, s_2$ )	Damping	Natural Response
$\zeta > 1$	Real and unequal	<i>Overdamped</i>	Sum of two decaying exponentials
$\zeta = 1$	Real and equal	<i>Critically damped</i>	Two faster decaying exponentials
$\zeta < 1$	Complex conjugates	<i>Underdamped</i>	Exponentially damped sinusoid

### Particular Solution

The particular solution is found by considering the full (non-homogeneous) differential equation, Eq. (5). If the forcing function is a constant, then  $y_P(t)$  is also a constant ( $K_3$ ), and hence

$\frac{dy_P}{dt} = 0 = \frac{d^2 y_P}{dt^2}$ . Substituting  $y_P$  into the differential equation yields:

$$\frac{d^2 y}{dt^2} + a \frac{dy}{dt} + b y(t) = 0 + a \cdot 0 + b y_P = f$$

Reducing the above expression provides the particular solution, which is the *forced response*

$$y_P = K_3 = \frac{f}{b}$$

Alternatively,  $K_3$  could have been determined from Eq. (6) and the final value  $y(\infty)$ .

### Initial Conditions

Initial conditions for  $y$  and its derivative are necessary to find  $K_1$  and  $K_2$ ; specifically needed are  $y(0)$  and  $\left. \frac{dy}{dt} \right|_{t=0}$ . A numerical value for  $\left. \frac{dy}{dt} \right|_{t=0}$  is generally found by re-applying KVL or KCL at  $t=0$ . Practically speaking, as the KVL or KCL is performed, the inductor voltage and capacitor current, respectively, are expressed as  $L \left. \frac{di_L}{dt} \right|_{t=0}$  and  $C \left. \frac{dv_C}{dt} \right|_{t=0}$ . The numerical value of  $\left. \frac{dy}{dt} \right|_{t=0}$  is then equated to an analytical derivative of  $y(t)$  determined from Eq. (6). The initial conditions for  $y(0)$  are found in the same manner as described for first-order differential equations.